

Toy Car Control Using Esp32 and Mobile(BLE)

Abstract—This document shows how to implement Mobile(BLE) controlled toy car using Esp32.

1 COMPONENTS REQUIRED:

- 1) Esp32 Deveopment Kit
- 2) Toy Car with Motors
- 3) L293D Motor Driver IC
- 4) Dabble app(Download from playstore)
- 5) Breadboard
- 6) Connecting Wires

2 CIRCUIT CONNECTION:

- 1) Refer the pin diagram of L293D motor driver IC

Esp32/IDE/Toycar_with_Mobile/Figures/pin.jpg

- 2) Connect Vcc1 pin to Vin pin on Esp32.
- 3) The input and enable pins(ENA, IN1, IN2, IN3, IN4 and ENB) of the L293D IC are connected to six Esp32 digital output pins(14, 16, 17, 18, 19 and 15).
- 4) Connect one motor to across OUT1 & OUT2 and the other motor across OUT3 & OUT4.
- 5) Connect external 9V battery to the Vcc2 pin of L293D motor driver IC
- 6) Connect external GND pin battery to the GND pin of L293D motor driver IC

Esp32/IDE/Toycar_with_Mobile/Figures/wiring.jpg

- 7) Go to arduino IDE and Write the the following code

Esp32/IDE/Toycar_with_Mobile/Codes

- 8) Click on Compile and Upload the code to "DOIT ESP32 DEVKITV1".
- 9) Now open Dabble app search for bluetooth devices and Select "MyEsp32" and connect it.
- 10) After connecting click on GamePad Icon and you will get control panel.